

```

module ripple_carry_adder_subtractor(S, C, V, A, B,
Op);
    output [3:0] S;    // The 4-bit sum/difference.
    output      C;    // The 1-bit carry/borrow status.
    output      V;    // The 1-bit overflow status.
    input  [3:0] A;    // The 4-bit augend/minuend.
    input  [3:0] B;    // The 4-bit addend/subtrahend.
    input      Op;    // The operation: 0 => Add,
1=>Subtract.

```

```

    wire C0; // The carry out bit of fa0, the carry
in bit of fa1.

```

```

    wire C1; // The carry out bit of fa1, the carry
in bit of fa2.

```

```

    wire C2; // The carry out bit of fa2, the carry
in bit of fa3.

```

```

    wire C3; // The carry out bit of fa2, used to
generate final carry/borrow.

```

```

    wire B0; // The xor'd result of B[0] and Op

```

```

    wire B1; // The xor'd result of B[1] and Op

```

```

    wire B2; // The xor'd result of B[2] and Op

```

```

    wire B3; // The xor'd result of B[3] and Op

```

```

    // Looking at the truth table for xor we see that

```

```

    // B xor 0 = B, and

```

```

    // B xor 1 = not(B).

```

```

    // So, if Op==1 means we are subtracting, then

```

```

    // adding A and B xor Op along with setting the
first

```

```

    // carry bit to Op, will give us a result of

```

```

    // A+B when Op==0, and A+not(B)+1 when Op==1.

```

```

    // Note that not(B)+1 is the 2's complement of B,
so

```

```

    // this gives us subtraction.
    xor(B0, B[0], Op);
    xor(B1, B[1], Op);
    xor(B2, B[2], Op);
    xor(B3, B[3], Op);
    xor(C, C3, Op);    // Carry = C3 for addition,
Carry = not(C3) for subtraction.
    xor(V, C3, C2);    // If the two most significant
carry output bits differ, then we have an overflow.

    full_adder fa0(S[0], C0, A[0], B0, Op);    //
Least significant bit.
    full_adder fa1(S[1], C1, A[1], B1, C0);
    full_adder fa2(S[2], C2, A[2], B2, C1);
    full_adder fa3(S[3], C3, A[3], B3, C2);    // Most
significant bit.
endmodule // ripple_carry_adder_subtractor

```